

İTÜ



Department of
Computer
Engineering

BLG 222E
Computer Organization
Report of Project-1

Experiment Date: 15.03.2018

Member's ID :

150150007
150150801
150150067
150140061

Member's Name :

Hatice Hüma Kalaycı
Alican Kurt
Refik Özgün Yeşildağ
Hakan Saraç

1. Introduction

The first project of Computer Organization course wants from us to design 8-bit and 16-bit registers, a general purpose register and an 16-bit IR address register. We designed the our systems as follows.

2. Equipments and Integrated Circuits

When preparing the circuits, we used these equipments in Logisim.

- 1-bit adders
- 2-select 8-data bits Multiplexer
- D flip-flops
- 8-bit registers
- 16-bit register

3. Experiment

3.1. Part-1

Control inputs and functions:

Enable	FunSel	Q*(Next State)	Function
0	∅	Q	Retain Value
1	00	0	Clear
1	01	Q+1	Increment
1	10	Q-1	Decrement
1	11	I(Input)	Load

Table 3.1.a Funsel control inputs and Functions

3.1.1. 8-bit Register

In this part we designed a 8-bit register which performs the clear, increment, decrement and load functions. To increment we added 1, and to decrement added (-1) 1111(2's complement of 1) to the our last state. Our FunSel inputs select the multiplexer output. We use enable input instead of clock for the D flip-flops.

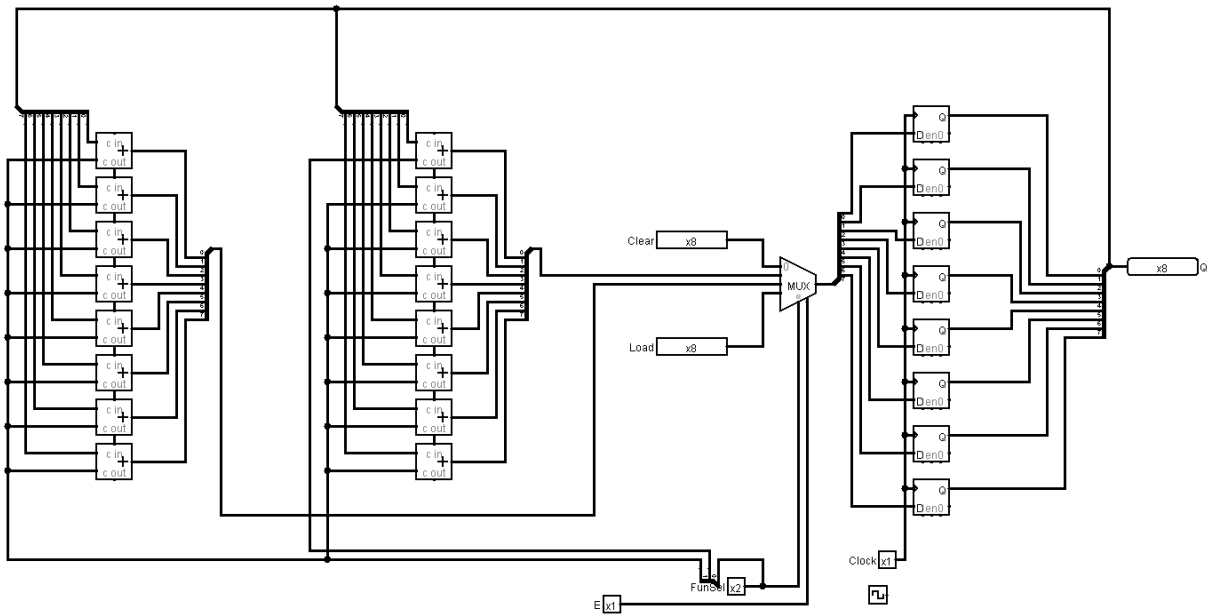


Figure 3.1.1.a 8-bit Register

3.1.2. 16-bit Register

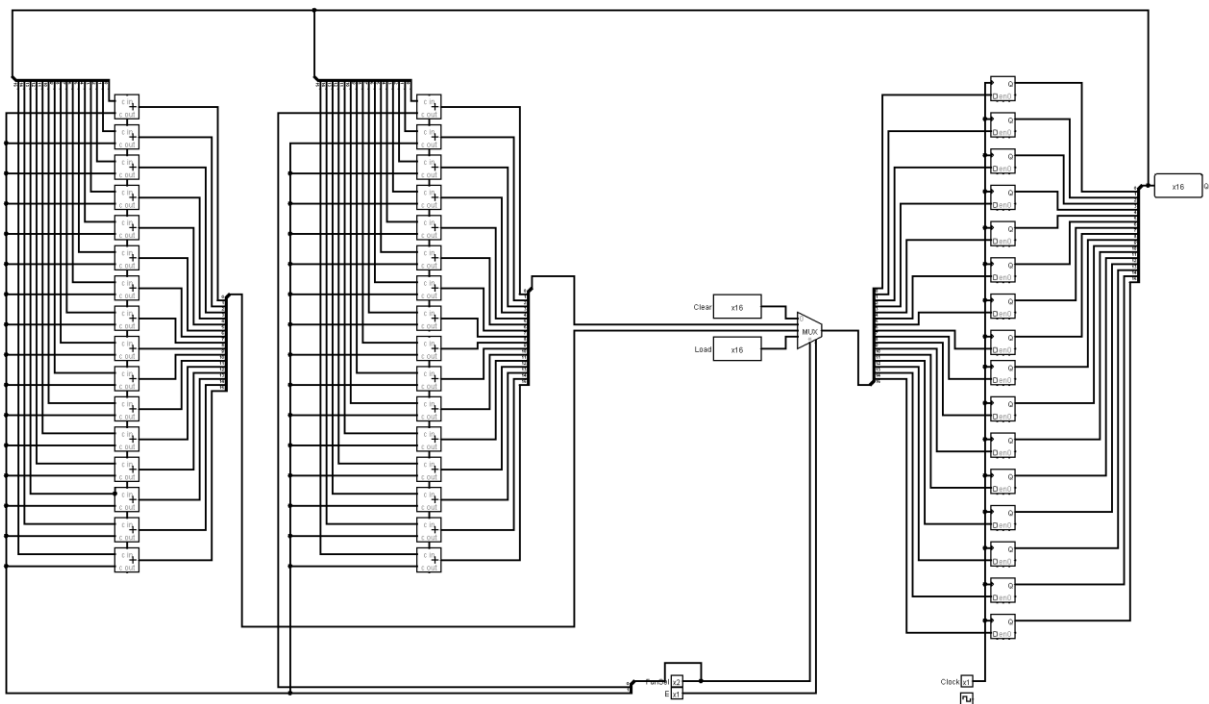


Figure 3.1.2.a 16-bit Register

In this step we use 16-bit instead of 8-bit. Its working principle is the same as 8-bit register.

3.2. Part-2

3.2.1. Part-2.a System of four 8-bit general purpose registers

Control inputs and functions:

Enable	FunSel	Q ⁺ (Next State)	Function
0	∅	Q	Retain Value
1	00	0	Clear
1	01	Q+1	Increment
1	10	Q-1	Decrement
1	11	I(Input)	Load

Table 3.2.1.a Funsel control inputs and Functions

OutAsel	Output(A)
00	R0
01	R1
10	R2
11	R3

OutBsel	Output(B)
00	R0
01	R1
10	R2
11	R3

Table 3.2.1.b Outsel control

Regsel	Enabled Registers
0000	-
0001	R3
0010	R2
0011	R2,R3
0100	R1
0101	R1,R3
0110	R1,R2
0111	R1,R2,R3
1000	R0
1001	R0,R3
1010	R0,R2
1011	R0,R2,R3
1100	R0,R1
1101	R0,R1,R3
1110	R0,R1,R2
1111	R0,R1,R2,R3

Table 3.2.1.c Outsel inputs and Outputs

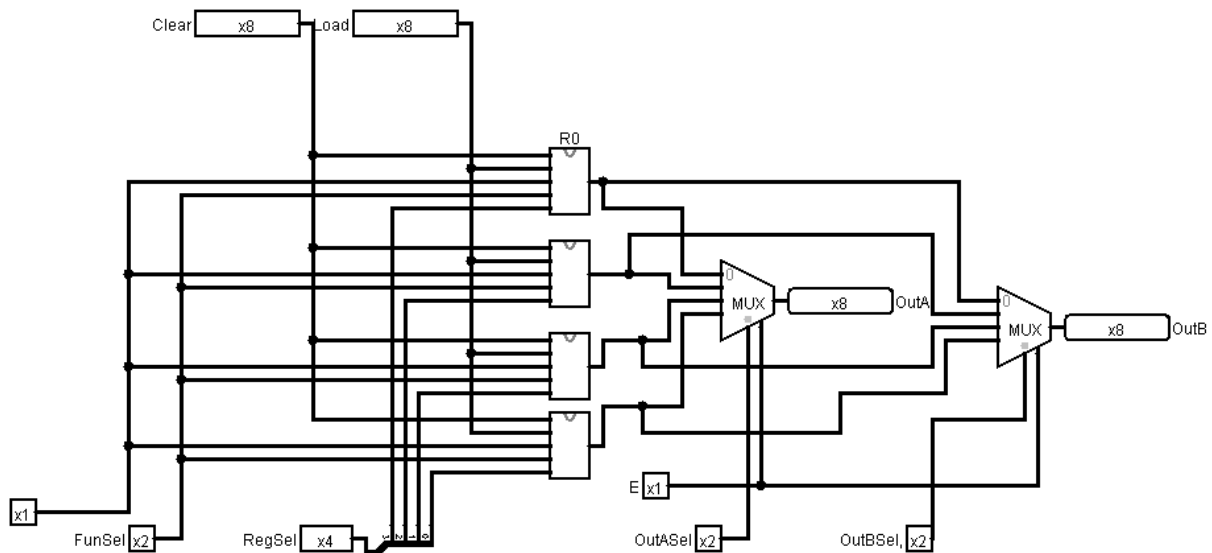


Figure 3.2.1.a 8-bit general purpose registers

We used 4 8-bit registers which is designed in part-1. Our inputs are clear, load, enable, FunSelect and RegSelect. Register Select decide which registers work (Table 3.2.1.c). FunSel inputs select the function (Table 3.2.1.a).

3.2.2. Part-2.b 8-bit adress registers

Control inputs and functions:

OutCsel	Output(C)
00	PC
01	PC
10	AR
11	SP

Table 3.2.2.a OutCsel control

This circuit performs the functions as Part2-a. But both 00 and 01 OutCsel inputs give the same result (PC). If OutCsel inputs are 10, we get AR's result and if they are 11, we get SP's result. Our output shows us the selected registers last state.

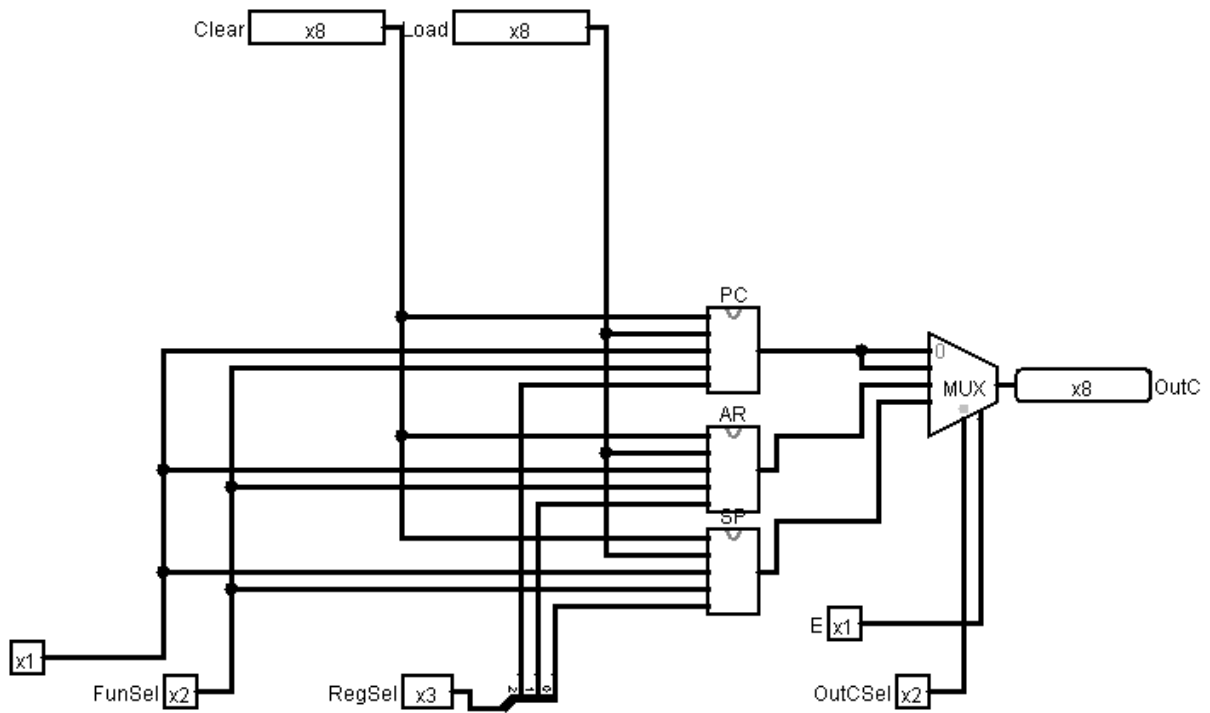


Figure 3.2.2.a 8-bit address registers:PC, AR, SP

3.2.3. Part-2.c 16-bit IR register

Control inputs and functions:

L	Enable	FunSel	IR ⁺	Function
Ø	0	Ø Ø	IR	Retain Value
1	1	11	IR(0-7)<-I	Load 0-7 bits
0	1	11	IR(8-15)<-I	Load 8-15 bits
Ø	1	00	0	Clear
Ø	1	01	IR+1	Increment
Ø	1	10	IR-1	Decrement

Table 3.2.3.a Characteristics of IR register

When we were designing the 16_bit IR register, we used the 16-bit register which is in the part-1. But our 8-bit load value replace registers 0-7 or 8-15 bit parts. Part replaced is selected by L input. If L is 0 our value replace 8-15 bit, otherwise 0-7 bit. When we decide the part, we use a multiplexer 1 select(L) and 16 data bits.

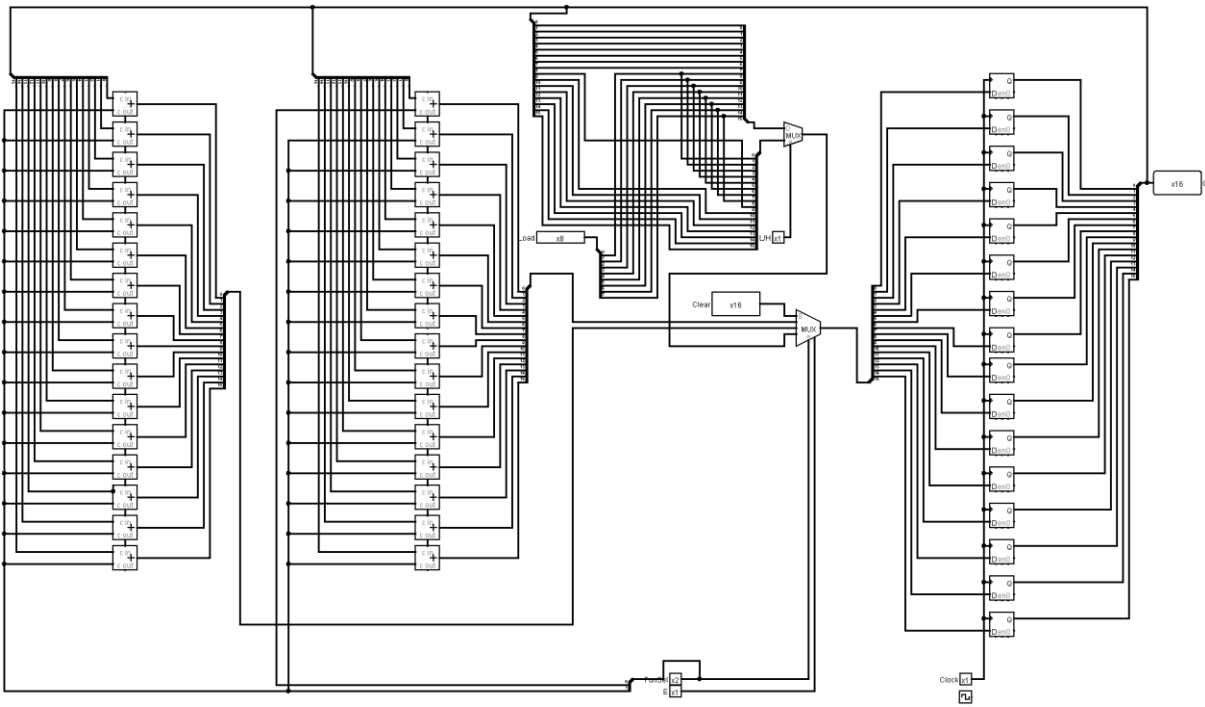


Figure 3.2.3.a 16-bit IR register

4. Conclusion

In this project we learned using Logisim Logic Simulator Software and designing and using registers by this program. All of team members ready for next subjects and projects.